

Multi-Stage Amplifier P1 Data Collection

Table 1: Multi-Stage DC Data

	<i>Calculated</i>	<i>Measured</i>		<i>Calculated</i>	<i>Measured</i>		<i>Calculated</i>
V_{CC}			$V_{CE_{Q1}}$			P_{Q1}	
			$V_{CE_{Q2}}$			P_{Q2}	
$R1$			V_{R1}			P_{R1}	
$R2$			V_{R2}			P_{R2}	
$R3$			V_{R3}			P_{R3}	
$R4$			V_{R4}			P_{R4}	
$R5$			V_{R5}			P_{R5}	
$R6$			V_{R6}			P_{R6}	
$R7$			V_{R7}			P_{R7}	
$R8$			V_{R8}			P_{R8}	
$R9$			V_{R9}			P_{R9}	
$R10$			V_{R10}			P_{R10}	
$R11$			V_{R11}			P_{R11}	
$R12$			V_{R12}			P_{R12}	

Table 2: Multi-Stage AC Data.

	<i>Calculated</i>	<i>Measured</i>		<i>Calculated</i>	<i>Measured</i>
Z_{in}			Z_{out}		
$V_{in_{PP}}$			$V_{out_{pp}}$		
ΔV_{Q1}			ΔV_{Q2}		
ΔV_{Total}					
$V_{in_{MAXp}}$			$V_{out_{MAXp}}$		

Table 3: Multi-Stage Low Frequency Response Data.

<i>Frequency Response Low, calculated capacitance values for 1KHz.</i>					
	<i>Calculated</i>		<i>Calculated</i>	<i>Std. Value</i>	<i>F_{cLOW} Std.V</i>
<i>R_{th}v_{C1}</i>		<i>C1</i>			
<i>R_{th}v_{C2}</i>		<i>C2</i>			
<i>R_{th}v_{C3}</i>		<i>C3</i>			
<i>R_{th}v_{C4}</i>		<i>C4</i>			
<i>R_{th}v_{C5}</i>		<i>C5</i>			
<i>R_{th}v_{C6}</i>		<i>C6</i>			
<i>Calculated F_{cLOW} using standard value capacitors F_{cLOW}Total :</i>					
<i>Sine-wave Analysis Measurement:</i>					
<i>F_{cLOW}Total :</i>					
<i>Square-wave Analysis Measurement:</i>					
<i>Tilt</i>		<i>PW</i>		<i>F_{cLOW}Total :</i>	
<i>Phase and dB Calculations and Measurements</i>					
	<i>Freq.</i>	<i>Calc.θ</i>	<i>Meas.θ</i>	<i>Calc. dB</i>	<i>Meas. dB</i>
<i>F_{cLOW}</i>					
<i>1st Octave</i>					
<i>1st Decade</i>					